

This question paper contains 4 printed pages.]

8475

Your Roll No.

B. Tech. (EEE) / I

A

Paper EEE-105

ADVANCED ELECTRONICS

Time : 3 Hours

Maximum Marks : 70

*(Write your Roll No. on the top immediately
on receipt of this question paper.)*


*Answer any **five** questions.*

Assume suitable missing data, if any.

1. (a) Define the parameters : Amplification factor, drain resistance and mutual conductance for JFET and derive the relationship among these factors. 7

(b) A transistor amplifier circuit shown in fig-1 has the following parameters $h_{ie} = 1500 \Omega$, $h_{fe} = 100$, $h_{re} = 4 \times 10^{-4}$ $h_{oe} = 4 \times 10^{-4}$ mho. Determine the ac input resistance of the amplifier and voltage gain. 7

[P.T.O.]

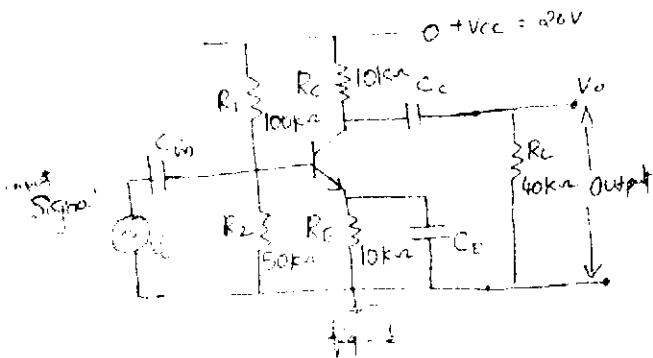

2. (a) Draw a self bias BJT circuit and derive the expression for $\delta(I_{CQ})$ and $\delta(V_{BE})$. Suggest a method for improving the stability of the circuit. 7
- (b) Explain the construction and working of a MOSFET with the help of a neat diagram. Draw the input and output characteristic of an Enhancement MOSFET in common source configuration. 7
3. (a) Explain different feedback configuration with example. 7
- (b) Explain in detail the working of R-C phase shift oscillator and derive the expression for frequency of oscillation. 7


4. (a) Using a neat sketch derive the expression for voltage gain, current gain and output resistance of a High frequency voltage Amplifier (BJT). (You can use either h-parameter model or π -model.) 7

(b) Explain the advantages of a negative feedback amplifier over positive feedback amplifier. 3

(c) An amplifier has gain $A = 60$ dB and output impedance $Z_o = 12.6$ K Ω . It is required to modify its output impedance to 600 Ω by applying negative feedback. Determine (a) the value of feedback factor (b) the percentage change in the overall gain for 10% change in gain of the basic amplifier. 4

5. (a) The efficiency of class C amplifier is much higher than class-A amplifier prove the above statement. 7

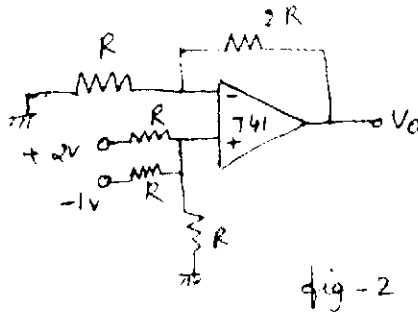(b) Explain the working of a push-pull amplifier with the help of a neat sketch. Also explain its advantages. 7



6. (a) Fig-2 shows a non inverting op-amp summer with $V_1 = 2V$ and $V_2 = -1V$. Calculate output voltage V_o . Derive the equations used. 7
- (b) Draw the circuit diagram of a low pass filter and high pass filter using op-amp and explain its working. 7
7. Write short notes on any two 7×2=14
- (i) 555 timer
 - (ii) Common base input and output characteristic
 - (iii) Schmitt trigger
 - (iv) Emitter coupled differential amplifier